

Precision reference bans precision resistors

Budge Ing, Maxim Integrated Products, Sunnyvale, CA

COMBINING A SWITCHED-CAPACITOR charge pump with a precision reference yields an inverted reference from a positive power supply (Figure 1). Unlike the more typical combination of a positive three-terminal reference and an op-amp inverter, this circuit performs accurate inversions without the need for precision resistors and a negative supply. The compact circuit requires only three surface-mount capacitors, and the ICs occupy tiny SOT-23 packages.

The charge-pump inverter, IC₂, delivers -5V by inverting the out-

put of a 5V precision reference, IC₁. IC₁ has an input range of 5.2 to 12.5V. Replacing IC₁ with a 2.5V reference that accepts 2.7 to 12.5V inputs produces a -2.5V output.

Output-voltage accuracy depends

partly on the initial accuracy of IC₁, which in this case is 1%. To determine the overall accuracy, you must add the error from the dropout voltage, which is less than 2 mV for 90 μ A of load current (Figure 2a). For a -2.5V output, the circuit draws quiescent current that ranges from 86 μ A for a 2.7V input to 105 μ A for a 12.5V input. For -5V outputs, the circuit draws 127 μ A for 5.2V inputs and 140 μ A for 12.5V inputs (Figure 2b). (DI #2368)

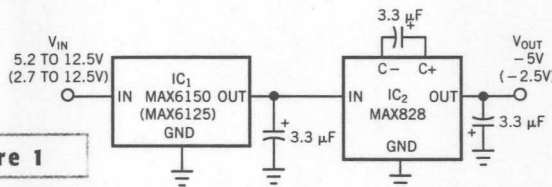


Figure 1

Combining a voltage reference and a charge-pump inverter forms a precision negative reference.

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 420


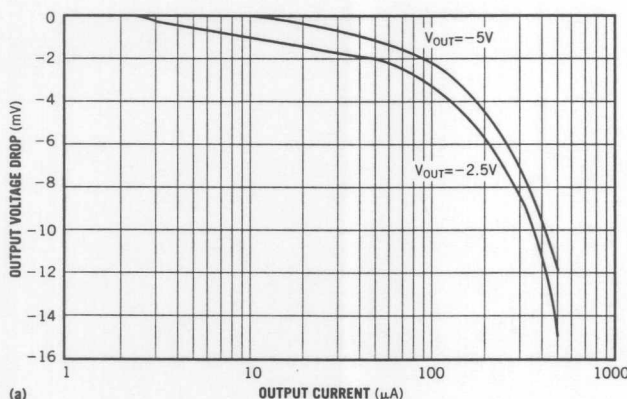


Figure 2

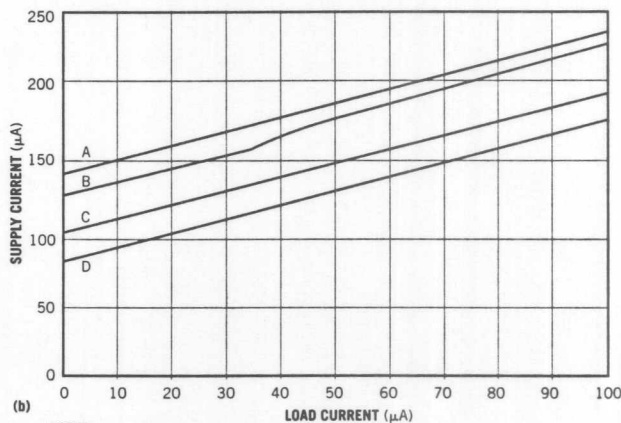

NOTES:
FOR TRACE A, VIN=12.5V, AND VOUT=-5V.
FOR TRACE B VIN=5.2V, AND VOUT=-5V.
FOR TRACE C, VIN=12.5V, AND VOUT=-2.5V.
FOR TRACE D, VIN=2.7V, AND VOUT=-2.5V.

For a -5V output, the dropout voltage is less than 2 mV at 90 μ A of output current (a). For a -5V output, quiescent current ranges from 127 to 140 μ A.

Easy method calculates comparator trip points

Virgil Lawrence, Micro Linear, San Jose, CA

USING MILLMAN'S THEOREM to calculate the resistor ratio reduces the time it takes to calculate the trip points on a comparator with hysteresis.

This method eliminates lengthy computations and substitutions. Using this resistor ratio, you select two resistors, assign convenient values, and then

calculate the third value.


Assume an inverting comparator with an upper limit of 4V and a lower trip voltage of 1.333V. The voltage on the in-

verting input needs to reach 1.333V for the output to switch to V_{CC} . Then, for the output to return to zero, the input voltage needs to reach 4V.

Millman's Theorem states that the sum of the products of the voltages times their respective conductances divided by the sum of the conductances gives the common junction-point voltage V_x (Figure 1). Or,

$$V_x = \frac{\sum V_N G_N}{\sum G_N}$$

Figure 1

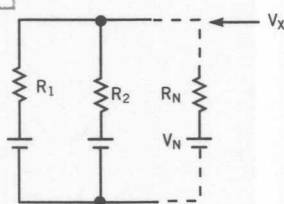

Millman's theorem states that the sum of the products of the voltages times their respective conductances divided by the sum of the conductances gives the common junction point voltage V_x .


where $G = 1/R$.

Using Millman's Theorem, with V_{CC} at the top of R_1 and R_F (Figure 2), set up the numerator with a Millman equation. Set up the denominator with another Millman equation when the output voltage is zero (with only one voltage source in the denominator). Assume that R_C is $\ll R_F$ and therefore negligible in the calculations. The resultant equation for the voltage ratio is:

$$\begin{aligned} \frac{V_{IN(HIGH)}}{V_{IN(LOW)}} &= \frac{\frac{\sum V_N G_N}{\sum G_N}}{\frac{\sum V_N G_N}{\sum G_N}} = \frac{\frac{12}{R_1} + \frac{12}{R_F}}{\frac{12}{R_1}} \\ &= \frac{R_F + R_1}{R_F} = \text{VOLTAGE RATIO.} \end{aligned}$$

This large fraction equals the voltage ratio $4/1.333 = 3$. First solve for R_F in terms of R_1 , and select R_1 in relation to R_F , such as $R_1 = 1 \text{ M}\Omega$, and $R_F = 500 \text{ k}\Omega$. Then solve for R_2 . The resistance ratio always equals the voltage ratio minus one. (DI #2372)

Figure 2

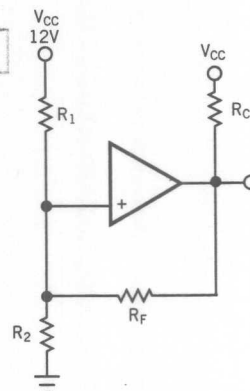

Using Millman's theorem, you can calculate that the voltage ratio of the trip points equals $(R_F + R_1)/R_F$.

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 421

If this can control this...

Think what it can do for you!

▶ A power company in Chile uses Z-World controllers to monitor and balance hundreds of megawatts in their 200kV and 500kV power distribution network. The controllers calculate instantaneous power and compensate for unexpected power fluctuations in far less than the required 30 ms!

Z-World's C-programmable BL1700 controller offers:

- 32 digital I/O lines. (You can add up to 256!)
- 4 full-duplex serial ports (networking and communication).
- 10 12-bit analog inputs connect directly to sensors.
- LCD and PLCBus™ ports provide expandability.

INNOVATION IN CONTROL TECHNOLOGY

Z-World offers a wide range of cost-effective C-programmable controllers and peripherals. Our integrated Dynamic C® development software provides real-time multi-tasking control.

2900 Spafford Street Davis CA 95616 USA Tel: 530.757.3737 Fax: 530.753.5141 www.zworld.com

ZWORLD

Call 1-888-362-3387
(toll free in U.S. and Canada)
for a free product catalog.